

W05 Sep 16 (D1) Matching sequences detector

Biplav Karna

USN Kongsberg


2019

Overview

- 1 Problem Description
- 2 State Diagram
- 3 Asm Diagram
- 4 Source Code
 - dff.vhd
 - one-bit-comparator.vhd
 - seq_detect_fsm.vhd
- 5 Simulation
 - Source Code
 - Output
- 6 Thanks


Matching Sequence Detector

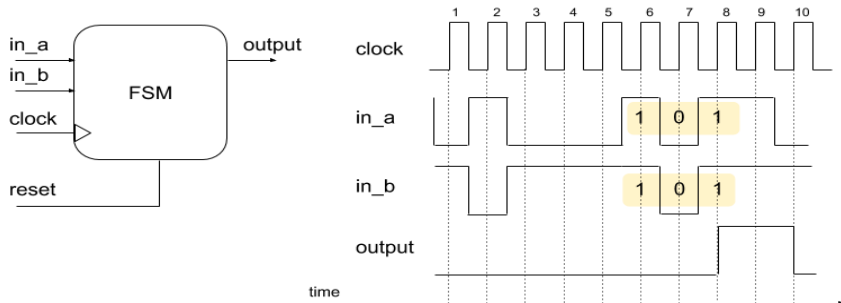Consider a two-inputs, one-output sequence detector that asserts its output whenever the two inputs have the same logic value during the last three consecutive clock cycles (see the example below).




1. Present a state diagram and ASM chart that represent the behaviour of this sequence detector.
2. Build a corresponding VHDL description and demonstrate the correct operation of your solution by simulation.

State Diagram

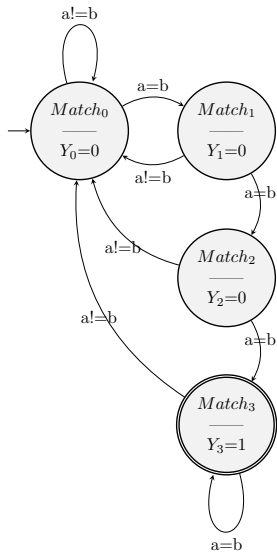

Asm Diagram

 

dff.vhd

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity dff is
    port (
        rst: in std_logic;
        clk: in std_logic;
        d: in std_logic;
        q: out std_logic
    );
end dff;

architecture dff_arch of dff is

begin

    process (rst , clk)
    begin
        if (rst = '1') then
            q <= '0';
        elsif ( rising_edge(clk) ) then
            q <= d;
        end if;
    end process;

end dff_arch;
```

one-bit-comparator.vhd

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity one_bit_comp is
    port (
        i0: in std_logic;
        i1: in std_logic;
        comp_out: out std_logic
    );
end one_bit_comp;

architecture one_bit_comp_arch of one_bit_comp is
begin
    comp_out <= (i0 and i1) or ( (not i0) and (not i1)) ;
end one_bit_comp_arch;
```

seq_detect_fsm.vhd

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity seq_det_fsm is
    port (
        clk: in std_logic;
        a,b: in std_logic;
        rst: in std_logic;
        result_out: out std_logic
    );
end seq_det_fsm;

architecture seq_det_fsm_arch of seq_det_fsm is

    signal fout_a,fout_b: std_logic;
    signal comp_result: std_logic;

    type seq_state_type is ( match0, match1, match2, match3);
    signal state_reg, state_next: seq_state_type;

begin

    a_register: entity work.dff(dff_arch) port map( rst =>rst, clk=>clk, d=>a, q=>fout_a);
    b_register: entity work.dff(dff_arch) port map( rst =>rst, clk=>clk, d=>b, q=>fout_b);
    comparator: entity work.one_bit_comp(one_bit_comp_arch) port map(i0 =>fout_a, i1=>
        fout_b, comp_out =>comp_result);

    — state register section

    process (rst, clk)
begin
```



```

if (rst = '1') then
    state_reg <= match0;
elsif ( rising_edge(clk) ) then
    state_reg <= state_next;
end if;

```

```

end process;

```

— *end state register section*

— *fsm next state section*

```

process (state_reg , comp_result)
begin
    case state_reg is
        when match0 =>

            if( comp_result = '1' ) then
                state_next <= match1;
            else
                state_next <= match0;
            end if;

        when match1 =>

            if( comp_result = '1' ) then
                state_next <= match2;
            else
                state_next <= match0;
            end if;

        when match2 =>

            if( comp_result = '1' ) then
                state_next <= match3;
            else

```

```

        state_next <= match0;
    end if;

    when match3 =>

        if( comp_result = '1' ) then
            state_next <= match3;
        else
            state_next <= match0;
        end if;

    end case;

end process;

-- end fsm next state section

-- output section

result_out <= '1' when (state_reg = match3) else
    '0';

-- output section
end seq_det_fsm_arch;
```

Source (seq_dectect_fsm_tb.vhd)

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity seq_det_fsm_tb is
end seq_det_fsm_tb;

architecture seq_det_fsm_tb_arch of seq_det_fsm_tb is

constant CLK_PERIOD: time :=10 ns;

signal clk,rst,a,b,result_out: std_logic;
begin

seq_detector: entity work.seq_det_fsm(seq_det_fsm_arch) port map ( clk=>clk , rst=>rst ,a=>
    a,b=>b, result_out=>result_out);

clock: process
begin
    clk <= '0' ;
    wait for CLK_PERIOD/2;
    clk <= '1' ;
    wait for CLK_PERIOD/2;
end process;

io_test: process
begin
    rst <= '0';
    a <= '0';
    b <= '0';
    rst <= '1';
```

```
wait until falling_edge (clk);
rst <= '0';
a <= '1';
b <= '0';

wait until falling_edge (clk);

a <= '1';
b <= '1';

wait until falling_edge (clk);
—wait for CLK_PERIOD * 4;

a <= '0';
b <= '0';

wait until falling_edge (clk);
a <= '1';
b <= '1';

wait until falling_edge (clk);
a <= '1';
b <= '1';


wait until falling_edge (clk);
a <= '1';
b <= '0';

wait until falling_edge (clk);
a <= '1';
b <= '1';

wait until falling_edge (clk);
a <= '0';
b <= '0';
```

```
        wait until falling_edge(clk);  
end process;  
  
end;
```

Output

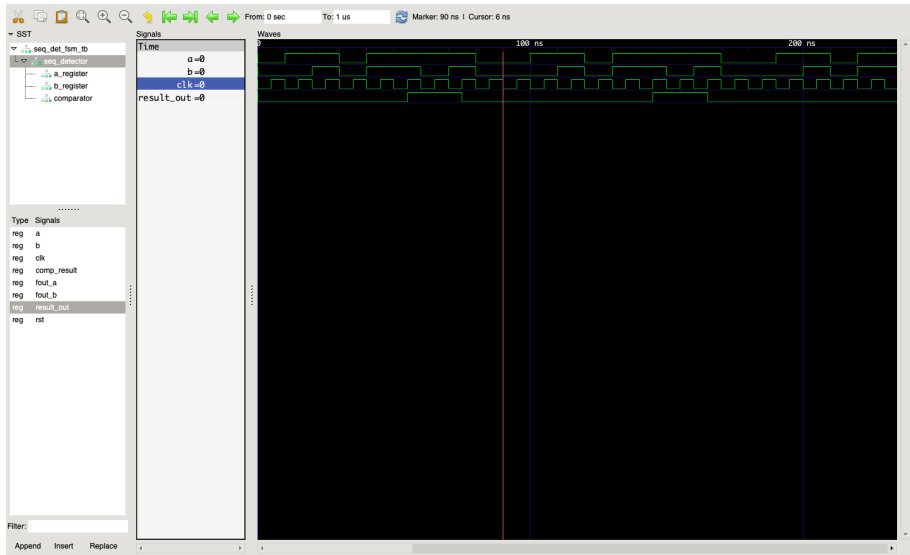

Thanks

